
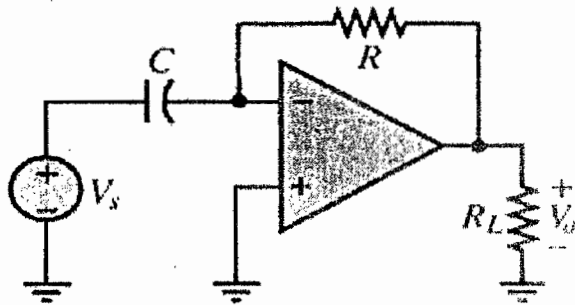


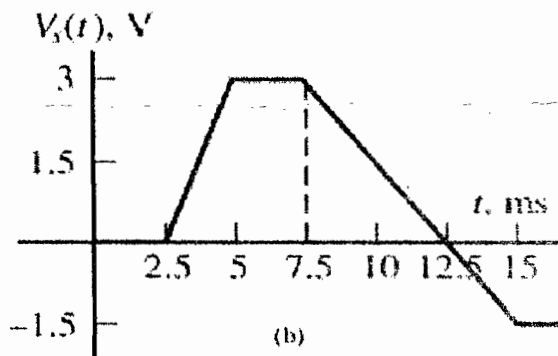1. Give a circuit shown in the part (a) of the following figure, where  $V_s$  is the input voltage and its waveform is given as part (b). Please calculate the output voltage  $V_o$  and plot your result on a new figure. The  $C=1\mu\text{F}$ ,  $R=10\text{K}\Omega$ ,  $R_L=1\text{K}\Omega$ . [20]





(a)




(b)

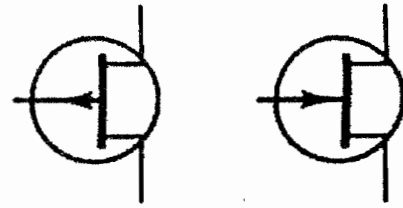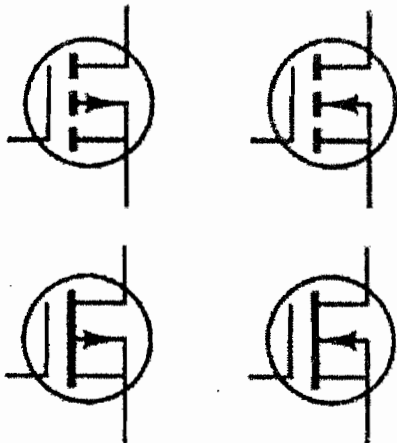2. Please give the complete name of the following symbols: [10]



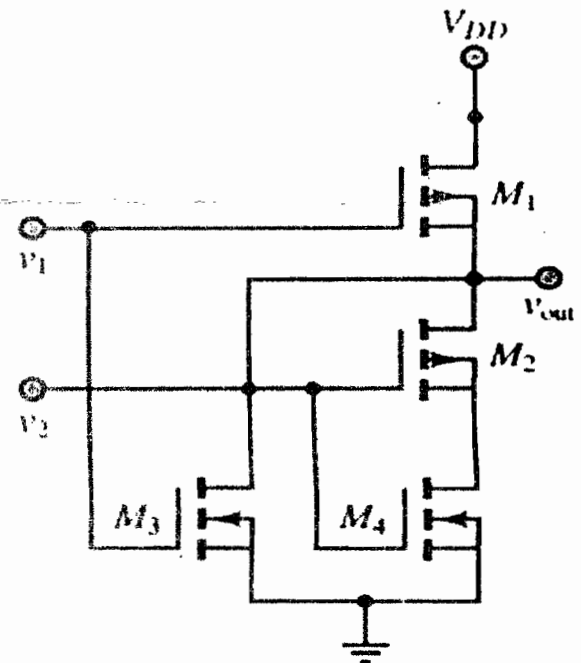3. Determine the logic function implemented by the CMOS gate of the following figure. Use the table below to summarize the behavior of the circuit. Note that the states of  $M_i$  must be filled with "on" or "off" to indicate the status of CMOS gates. The output voltage,  $v_{out}$ , will be the real voltage with respect to the input voltages. [20]





$v_1$	$v_2$	State of $M_1$	State of $M_2$	State of $M_3$	State of $M_4$	$V_{out}$
0V	0V					
0V	5V					
5V	0V					
5V	5V					

本試題採  
雙面印刷


第 / 頁共 2 頁

4. Please answer the following questions:

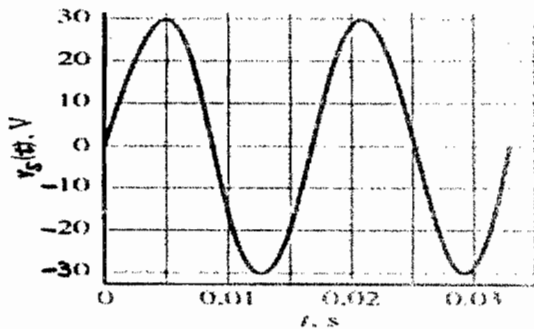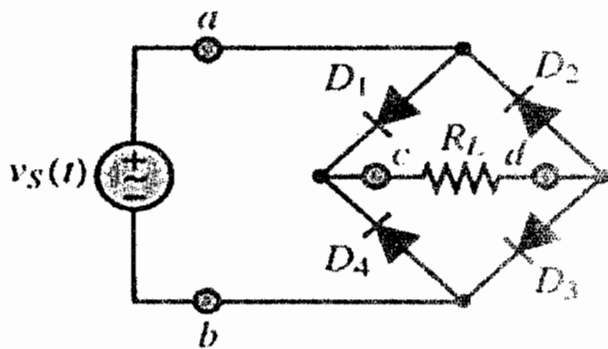- (a) Please describe the meaning of depletion region of a PN diode. [5]
- (b) Give a bridge rectifier circuit shown at the top part of the following figure. If the input voltage,  $v_s(t)$ , is shown in the lower part of the figure. Please draw the output voltage,  $v_L(t)$ , and the current  $i_L(t)$  of the load resistor  $R_L$  with respect to the input voltage. [10]



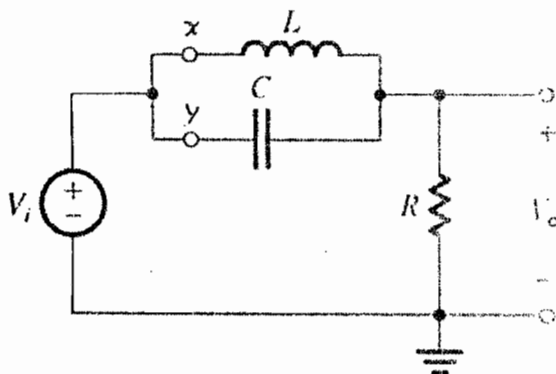5. Give a "Notch" filter, shown as follow. The natural frequency is  $\omega_0 = \sqrt{LC}$ . [15]



a. Please show the transfer function.


$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s^2 + \omega_0^2)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$

b. Please give the value of a.

c. Please show the value of Q.

6. Give a common-gate (CG) circuit. An input signal,  $v_{sig}$ , is applied to the source, and the output is taken at the drain of MOSFET with the gate forming a common terminal between the input and output ports. Please answer the following questions:[20]

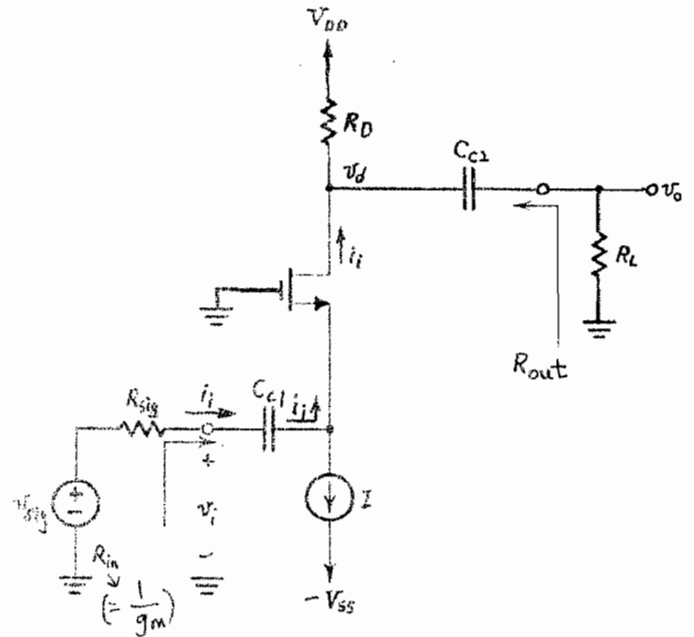- a. Please give the voltage of  $v_i$  with respect to  $v_{sig}$ ,  $g_m$  and resistors.
- b. Please derive the  $i_i$  with respect to  $g_m$  and  $v_i$ .
- c. Please find out the output voltage,  $v_o$ , with respect to  $g_m$ ,  $v_i$  and resistors.
- d. Please give the open-circuit gain,  $A_{vo}$ .
- e. Please give the output resistance,  $R_{out}$ .



本試題採  
双面印刷

第2頁共2頁